



SIMON FRASER
UNIVERSITY

Department of Engineering Science
Faculty of Applied Science

Course Code:	ENSC 252 1207
Course Title:	Fundamentals of Digital Logic
Semester Code:	Fall 2020 1207

Instructor:	Prof. Anita Tino
-------------	------------------

Asst/Lab No. :	5
Asst/Lab Title:	Distress Box

Submission Date:	November 15 2020
------------------	------------------

Student Name:	Devon Burnham
SFU ID:	301394066
Signature*:	(Devon Burnham)

*By signing above, I certify that the contribution made to this lab/assignment is solely mine and confirm that all work completed is my own. Any suspicion of plagiarism and/or copying will result in an investigation in the ENSC department. A mark of zero or F may be assigned, and depending on the level of severity, an FD grade on my transcript and/or expulsion from the school, according SFU's Code of Academic Integrity found online at <http://www.sfu.ca/policies/gazette/student/s10-01.html>

Sequencer VHDL Code
(genericized to support any data width and number of states)

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY sequencer IS
    GENERIC (
        data_width : INTEGER := 6;
        N : INTEGER := 33);
    PORT (
        clk : IN STD_LOGIC;
        reset : IN STD_LOGIC;
        count : OUT unsigned(data_width-1 DOWNT0 0));
END sequencer;

ARCHITECTURE behaviour OF sequencer IS

    SIGNAL countSig : unsigned(data_width-1 DOWNT0 0);

BEGIN
    PROCESS (reset, clk) IS
    BEGIN
        IF (reset = '1') THEN
            countSig <= to_unsigned(N, data_width);
        ELSIF (rising_edge(clk)) THEN
            IF (countSig = to_unsigned(0, data_width)) THEN
                countSig <= to_unsigned(N, data_width);
            ELSE
                countSig <= countSig - to_unsigned(1, data_width);
            END IF;
        ELSE
            countSig <= countSig;
        END IF;
    END PROCESS;

    count <= countSig;

END behaviour;
```

SOS Sequencer Testbench Code

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY tb_sequencer1 IS
END ENTITY;

ARCHITECTURE test OF tb_sequencer1 IS

    COMPONENT sequencer IS
        GENERIC (
            data_width : INTEGER := 6;
            N : INTEGER := 33);
        PORT (
            clk : IN STD_LOGIC;
            reset : IN STD_LOGIC;
            count : OUT unsigned(data_width - 1 DOWNTO 0));
    END COMPONENT;

    CONSTANT HALF_PERIOD : TIME := 10 ns;
    CONSTANT PERIOD : TIME := 20 ns;

    SIGNAL sigclk : STD_LOGIC := '1';
    SIGNAL sigreset : STD_LOGIC;
    SIGNAL sigcount : unsigned(5 DOWNTO 0);

BEGIN

    DUT : sequencer [GENERIC MAP(6, 33)]
    PORT MAP(sigclk, sigreset, sigcount);

    --to cycle clk for the duration of the test
    sigclk <= NOT sigclk AFTER HALF_PERIOD;

    PROCESS IS
    BEGIN

        --reset
        sigreset <= '1';
        WAIT FOR HALF_PERIOD;
        sigreset <= '0';
        WAIT;


    END PROCESS;

END ARCHITECTURE;
```

6-wide, 34 states

SOS Sequencer Waveforms


reset

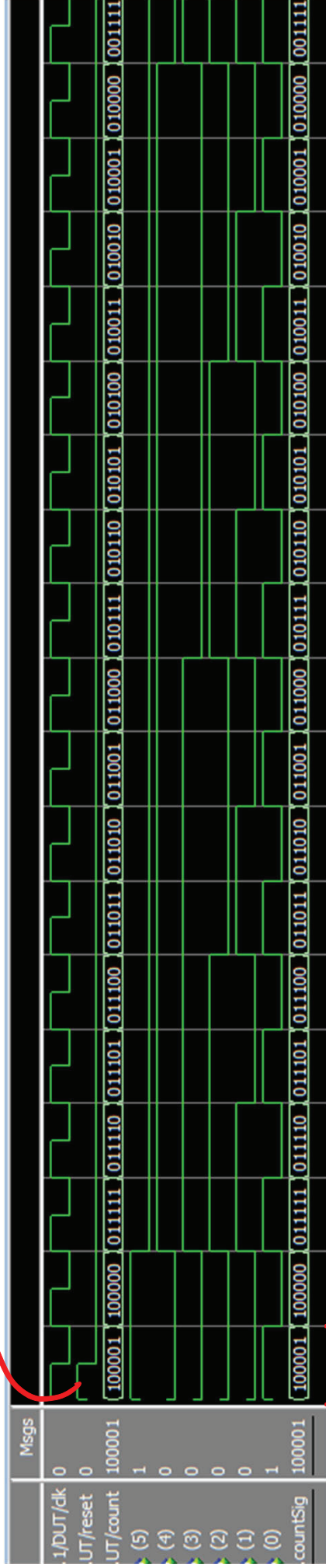

33

A reset input at the beginning starts off the process, then on every rising edge of clk, count decreases by one. Count has been expanded in these first waveforms to show the details of decrementing, but hereafter it may be collapsed to the single-lined representation, e.g. 100001. In this testbench, it begins at 100001 (33), and decrements down to 000000, at which point it underflows and restarts at 100001.

underflow

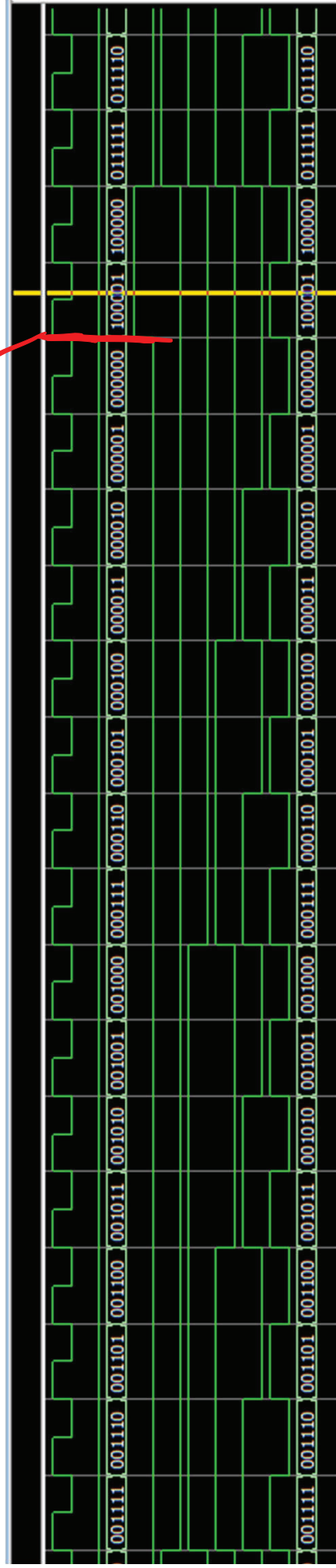

DEVO Sequencer Testbench Code

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY tb_sequencer2 IS
END ENTITY;

ARCHITECTURE test OF tb_sequencer2 IS

    COMPONENT sequencer IS
        GENERIC (
            data_width : INTEGER := 6;
            N : INTEGER := 33);
        PORT (
            clk : IN STD_LOGIC;
            reset : IN STD_LOGIC;
            count : OUT unsigned(data_width - 1 DOWNTO 0));
    END COMPONENT;

    CONSTANT HALF_PERIOD : TIME := 10 ns;
    CONSTANT PERIOD : TIME := 20 ns;

    SIGNAL sigclk : STD_LOGIC := '1';
    SIGNAL sigreset : STD_LOGIC;
    SIGNAL sigcount : unsigned(5 DOWNTO 0);

BEGIN

    DUT : sequencer GENERIC MAP(6, 43)
    PORT MAP(sigclk, sigreset, sigcount);

    --to cycle clk for the duration of the test
    sigclk <= NOT sigclk AFTER HALF_PERIOD;

    PROCESS IS
    BEGIN

        --reset
        sigreset <= '1';
        WAIT FOR HALF_PERIOD;
        sigreset <= '0';
        WAIT;
    END PROCESS;

END ARCHITECTURE;
```

44 states
(only difference vs. SOS sequencer)

Msgs																																														
...	...2DUT/dk	1																																												
...	...UT/reset	0																																												
...	...UT/count	100000	101011	101010	101001	101000	100111	100110	100101	100100	100011	100010	100001	100000	011111	011110	011101	011100	011011	011010	011001	011000	010111	010110	010101	010100	010011	010010	010001	010000	001111	001110	001101	001100	001011	001010	001001	001000	000111	000110	000101	000100	000011	000010	000001	000000
...	(5)	1																																												
...	(4)	0																																												
...	(3)	0																																												
...	(2)	0																																												
...	(1)	0																																												
...	(0)	0																																												
...	...countSig	100000	101011	101010	101001	101000	100111	100110	100101	100100	100011	100010	100001	100000	011111	011110	011101	011100	011011	011010	011001	011000	010111	010110	010101	010100	010011	010010	010001	010000	001111	001110	001101	001100	001011	001010	001001	001000	000111	000110	000101	000100	000011	000010	000001	000000

This set of waveforms is identical to the previous set of waveforms, the sole difference is that it begins and underflows to 101011 (43), instead of 100001 (33). This is because the morse code for DEVO, the first 4 letters of my name (Devon), is 44 units of time long, including the 7 units at the end of each transmission to signify the end of a word.

	0	1	2	522	523</
--	---	---	---	---	---	---	---	---	---	---	----	----	----	----	-----	-----	-----	-----	-------

Decoder VHDL Code
(genericized to support any decoding key)

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY decoder IS
    GENERIC (
        morse : STD_LOGIC_VECTOR);
    PORT (
        seq : IN unsigned(5 DOWNTO 0);
        WaveOut : OUT STD_LOGIC);
END ENTITY;

ARCHITECTURE behaviour OF decoder IS
BEGIN
    WaveOut <= morse((morse'length - 1) - to_integer(seq));
END ARCHITECTURE;
```

.

SOS Decoder Testbench Code

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY tb_decoder1 IS
END ENTITY;

ARCHITECTURE test OF tb_decoder1 IS

    COMPONENT decoder IS
        GENERIC (
            morse : STD_LOGIC_VECTOR);
        PORT (
            seq : IN unsigned;
            WaveOut : OUT STD_LOGIC);
    END COMPONENT;

    CONSTANT HALF_PERIOD : TIME := 10 ns;
    CONSTANT PERIOD : TIME := 20 ns;

    SIGNAL sigseq : unsigned(5 DOWNTO 0);
    SIGNAL sigwave : STD_LOGIC;

BEGIN

    DUT : decoder GENERIC MAP("1010100011101110111000101010000000")
    PORT MAP(sigseq, sigwave);

    PROCESS IS
    BEGIN


        FOR i IN 33 DOWNTO 0 LOOP
            sigseq <= to_unsigned(i, 6);
            WAIT FOR HALF_PERIOD;
        END LOOP;

        WAIT;
    END PROCESS;

END ARCHITECTURE;
```

Morse code for "SOS"

SOS Decoder Testbench Waveforms

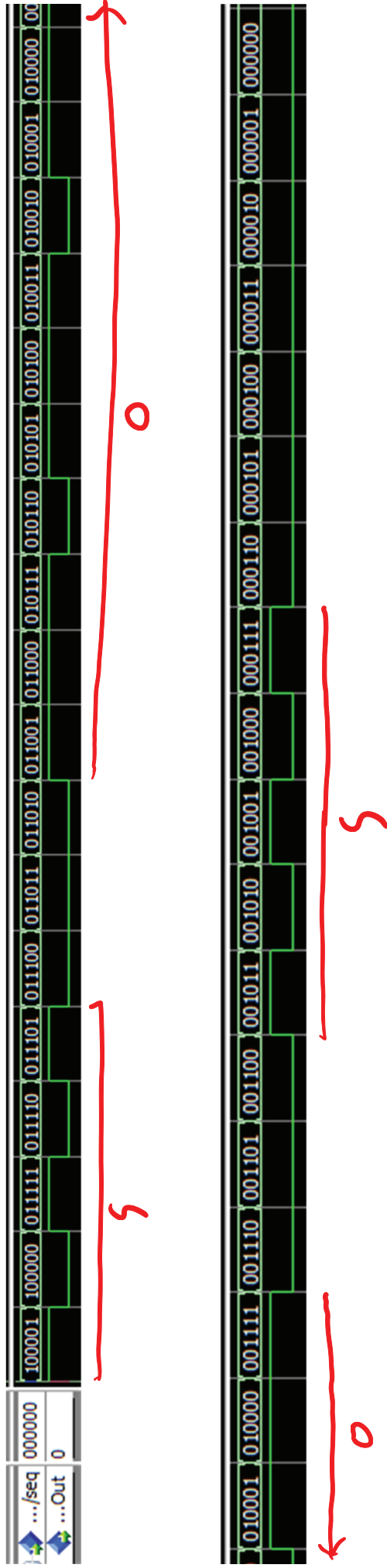

This waveform provides an unsigned signal decrementing from 33 down to 0, and the expected output is the morse code for "SOS", which is what is produced. The waveform has been split here for easier viewing; the first waveform ends at 010000 and the second begins a little earlier at 010001. Nevertheless, the expected pattern of SOS is clearly visible in the output.

DEVO Decoder Testbench Code

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY tb_decoder2 IS
END ENTITY;

ARCHITECTURE test OF tb_decoder2 IS

    COMPONENT decoder IS
        GENERIC (
            morse : STD_LOGIC_VECTOR);
        PORT (
            seq : IN unsigned;
            WaveOut : OUT STD_LOGIC);
    END COMPONENT;

    CONSTANT HALF_PERIOD : TIME := 10 ns;
    CONSTANT PERIOD : TIME := 20 ns;

    SIGNAL sigseq : unsigned(5 DOWNTO 0);
    SIGNAL sigwave : STD_LOGIC;

BEGIN

    DUT : decoder GENERIC MAP("11101010001000101010111000111011101110000000")
    PORT MAP(sigseq, sigwave);

    PROCESS IS
    BEGIN


        FOR i IN 43 DOWNTO 0 LOOP
            sigseq <= to_unsigned(i, 6);
            WAIT FOR HALF_PERIOD;
        END LOOP;

        WAIT;
    END PROCESS;

END ARCHITECTURE;
```

Morse for "DEVO"
(only difference vs. SOS decoder)

DEVO Decoder Testbench Waveforms

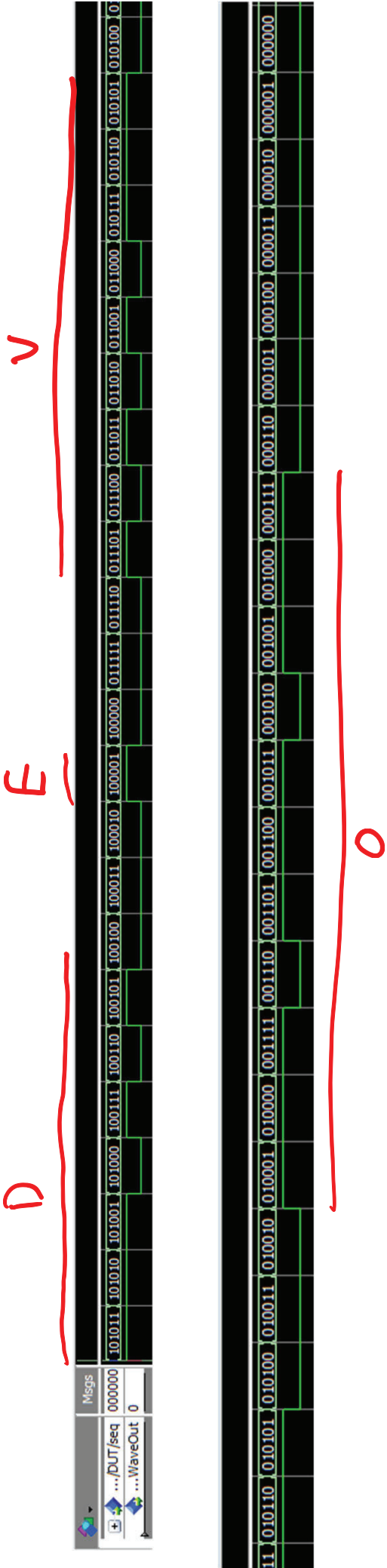

This waveform is the same as the previous one, except it decodes a pattern of 44 down to 0 into the morse code representation for DEVO. This is successfully produced, as seen above.

Box VHDL Code
(genericized to support any repeating output)

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY box IS
    GENERIC (
        data_width : INTEGER := 6;
        N : INTEGER := 33;
        morse : STD_LOGIC_VECTOR);
    PORT (
        clk : IN STD_LOGIC;
        reset : IN STD_LOGIC;
        enable : IN STD_LOGIC;
        code_out : OUT STD_LOGIC);
END ENTITY;

ARCHITECTURE structural OF box IS

    COMPONENT sequencer IS
        GENERIC (
            data_width : INTEGER := 6;
            N : INTEGER := 33);
        PORT (
            clk : IN STD_LOGIC;
            reset : IN STD_LOGIC;
            count : OUT unsigned(data_width-1 DOWNTO 0));
    END COMPONENT;

    COMPONENT decoder IS
        GENERIC (
            morse : STD_LOGIC_VECTOR);
        PORT (
            seq : IN unsigned(data_width-1 DOWNTO 0);
            WaveOut : OUT STD_LOGIC);
    END COMPONENT;

    SIGNAL countSig : unsigned(data_width-1 DOWNTO 0);
    SIGNAL waveSig : STD_LOGIC;

BEGIN

    sequ : sequencer GENERIC MAP(data_width, N)
    PORT MAP(clk, reset, countSig);
    dec : decoder GENERIC MAP(morse)
    PORT MAP(countSig, waveSig);

    code_out <= waveSig WHEN (enable = '1') ELSE
        '0';

END ARCHITECTURE;
```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY tb_box1 IS
END ENTITY;

ARCHITECTURE test OF tb_box1 IS

    COMPONENT box IS
        GENERIC (
            data_width : INTEGER := 6;
            N : INTEGER := 33;
            morse : STD_LOGIC_VECTOR);
        PORT (
            clk : IN STD_LOGIC;
            reset : IN STD_LOGIC;
            enable : IN STD_LOGIC;
            code_out : OUT STD_LOGIC);
    END COMPONENT;

    CONSTANT HALF_PERIOD : TIME := 10 ns;
    CONSTANT PERIOD : TIME := 20 ns;

    SIGNAL sigclk : STD_LOGIC := '1';
    SIGNAL sigreset : STD_LOGIC;
    SIGNAL sigenable : STD_LOGIC;
    SIGNAL sigcode_out : STD_LOGIC;

BEGIN

    DUT : box GENERIC MAP(6, 33, "1010100011101110111000101010000000")
    PORT MAP(sigclk, sigreset, sigenable, sigcode_out);

    --to cycle clk for the duration of the test
    sigclk <= NOT sigclk AFTER HALF_PERIOD;

    PROCESS IS
    BEGIN

        --reset
        sigreset <= '1';
        sigenable <= '1';
        WAIT FOR HALF_PERIOD;
        sigreset <= '0';

        WAIT FOR PERIOD * 34; --to ensure looping works

        --reset
        sigreset <= '1';
        sigenable <= '0';
        WAIT FOR PERIOD;
        sigreset <= '0';

        wait;


    END PROCESS;

END ARCHITECTURE;


```

34 states, morse for
"sos"


SOS Box Testbench Waveforms

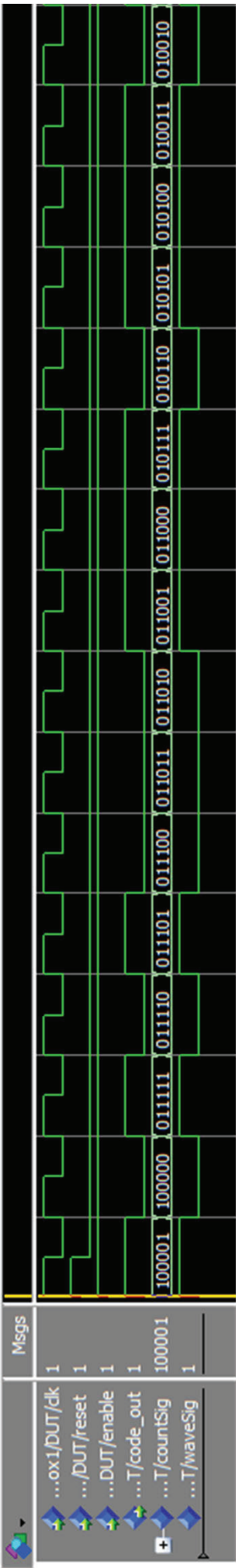

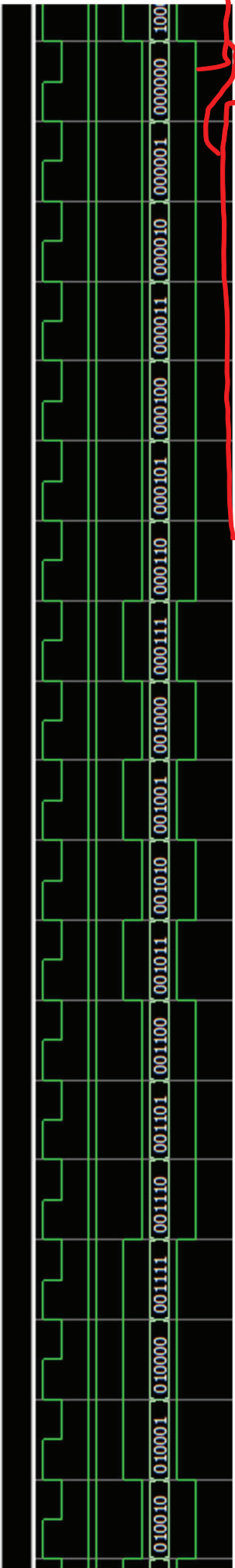With only clk and reset inputs, this circuit produces the correct waveform for the morse code representation of SOS, with the rising edge of the clk signal corresponding to the next unit of time.



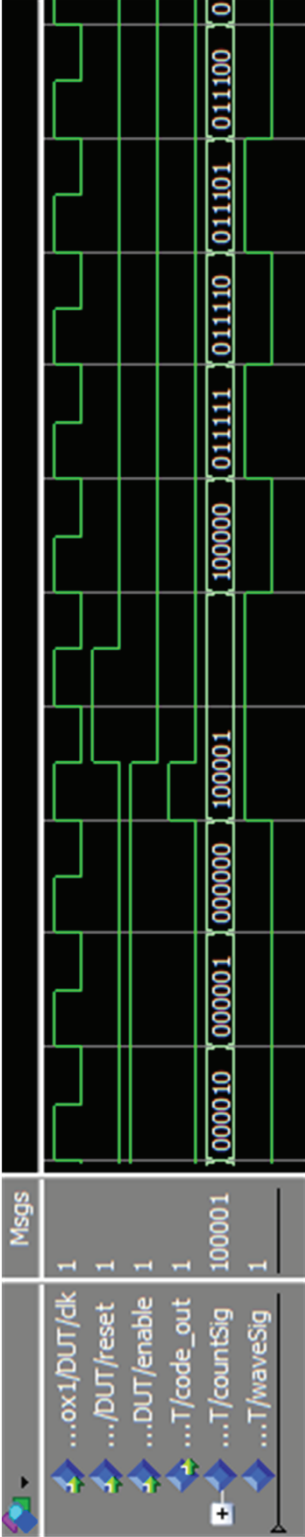Visible at the end of this waveform is the beginning of the next transmission, after the 7 spaces it resets to state 33 and begins to transmit 'S'. This is swiftly interrupted to demonstrate the asynchronous reset and enable/disable functionality.



This screenshot shows how setting enable to '0' suppresses the output, regardless of what waveSig is showing.

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY tb_box2 IS
END ENTITY;

ARCHITECTURE test OF tb_box2 IS

    COMPONENT box IS
        GENERIC (
            data_width : INTEGER := 6;
            N : INTEGER := 33;
            morse : STD_LOGIC_VECTOR);
        PORT (
            clk : IN STD_LOGIC;
            reset : IN STD_LOGIC;
            enable : IN STD_LOGIC;
            code_out : OUT STD_LOGIC);
    END COMPONENT;

    CONSTANT HALF_PERIOD : TIME := 10 ns;
    CONSTANT PERIOD : TIME := 20 ns;

    SIGNAL sigclk : STD_LOGIC := '1';
    SIGNAL sigreset : STD_LOGIC;
    SIGNAL sigenable : STD_LOGIC;
    SIGNAL sigcode_out : STD_LOGIC;

BEGIN

    DUT : box GENERIC MAP(6, 43, "11101010001000101010111000111011101110000000")
    PORT MAP(sigclk, sigreset, sigenable, sigcode_out);

    --to cycle clk for the duration of the test
    sigclk <= NOT sigclk AFTER HALF_PERIOD;

    PROCESS IS
    BEGIN

        --reset
        sigreset <= '1';
        sigenable <= '1';
        WAIT FOR HALF_PERIOD;
        sigreset <= '0';

        WAIT FOR period * 44; --to ensure looping works

        --reset
        sigreset <= '1';
        sigenable <= '0';
        WAIT FOR period;
        sigreset <= '0';


    wait;
    END PROCESS;

END ARCHITECTURE;



```

44 states, morse for
"DEVO" (only difference
vs. box1)

DEVO Box Testbench Waveforms

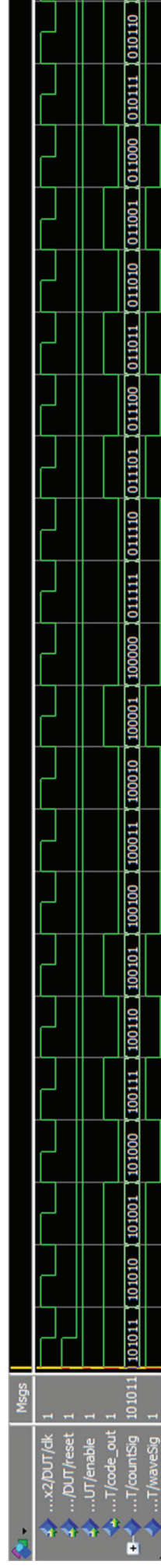

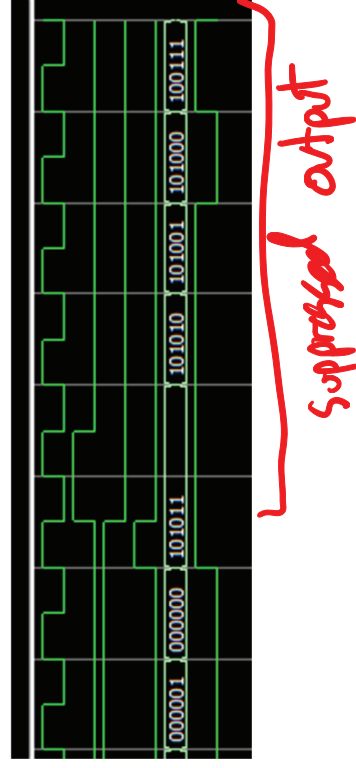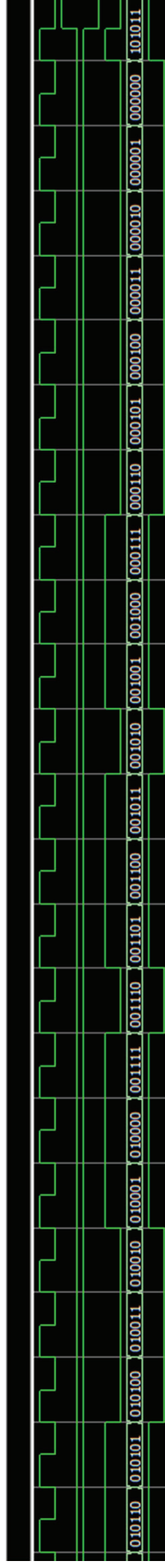This waveform has identical characteristics to the previous waveform, except it produces the morse code for DEVO instead of SOS. Reset, clk, and enable all work the same as before, as shown in these screenshots.



Distress Box VHDL Code

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY distress_box IS
    PORT (
        clk : IN STD_LOGIC;
        reset : IN STD_LOGIC;
        enable : IN STD_LOGIC;
        sel : IN STD_LOGIC;
        code_out : OUT STD_LOGIC
    );
END ENTITY;

ARCHITECTURE structural OF distress_box IS

    COMPONENT box IS
        GENERIC (
            data_width : INTEGER := 6;
            N : INTEGER := 33;
            morse : STD_LOGIC_VECTOR
        );
        PORT (
            clk : IN STD_LOGIC;
            reset : IN STD_LOGIC;
            enable : IN STD_LOGIC;
            code_out : OUT STD_LOGIC
        );
    END COMPONENT;

    SIGNAL code1 : STD_LOGIC;
    SIGNAL code2 : STD_LOGIC;

BEGIN

    b1 : box GENERIC MAP(6, 33, "1010100011101110111000101010000000")
        PORT MAP(clk, reset, enable, code1);
    b2 : box GENERIC MAP(6, 43, "11101010001000101010111000111011101110000000")
        PORT MAP(clk, reset, enable, code2);

    code_out <= code1 WHEN (sel = '0') ELSE
        code2;

END ARCHITECTURE;
```

SOS

DEVO

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
ENTITY tb_distress_box IS
END ENTITY;
ARCHITECTURE test OF tb_distress_box IS
    COMPONENT distress_box IS
        PORT (
            clk : IN STD_LOGIC;
            reset : IN STD_LOGIC;
            enable : IN STD_LOGIC;
            sel : IN STD_LOGIC;
            code_out : OUT STD_LOGIC );
    END COMPONENT;

    CONSTANT HALF_PERIOD : TIME := 10 ns;
    CONSTANT PERIOD : TIME := 20 ns;

    SIGNAL sigclk : STD_LOGIC := '1';
    SIGNAL sigreset : STD_LOGIC;
    SIGNAL sigenable : STD_LOGIC;
    SIGNAL sigsel : STD_LOGIC;
    SIGNAL sigcode_out : STD_LOGIC;

```

Distress Box Testbench Code
(some linebreaks removed to fit on one page)

```

BEGIN
    DUT : distress_box PORT MAP(sigclk, sigreset, sigenable, sigsel, sigcode_out);
    --to cycle clk for the duration of the test
    sigclk <= NOT sigclk AFTER HALF_PERIOD;

    PROCESS IS
    BEGIN
        --reset
        sigreset <= '1';
        sigenable <= '1';
        sigsel <= '0';
        WAIT FOR HALF_PERIOD;
        sigreset <= '0';

        WAIT FOR period * 34; --to ensure looping works

        --reset
        sigreset <= '1';
        sigenable <= '0';
        WAIT FOR HALF_PERIOD;
        sigreset <= '0';

        WAIT FOR period * 5;


        --reset
        sigreset <= '1';
        sigenable <= '1';
        sigsel <= '1';
        WAIT FOR HALF_PERIOD;
        sigreset <= '0';

        WAIT FOR period * 44; --to ensure looping works


        --reset
        sigreset <= '1';
        sigenable <= '0';
        WAIT FOR HALF_PERIOD;
        sigreset <= '0';
        wait;
    END PROCESS;
END ARCHITECTURE;

```

Distress Box Testbench Waveforms

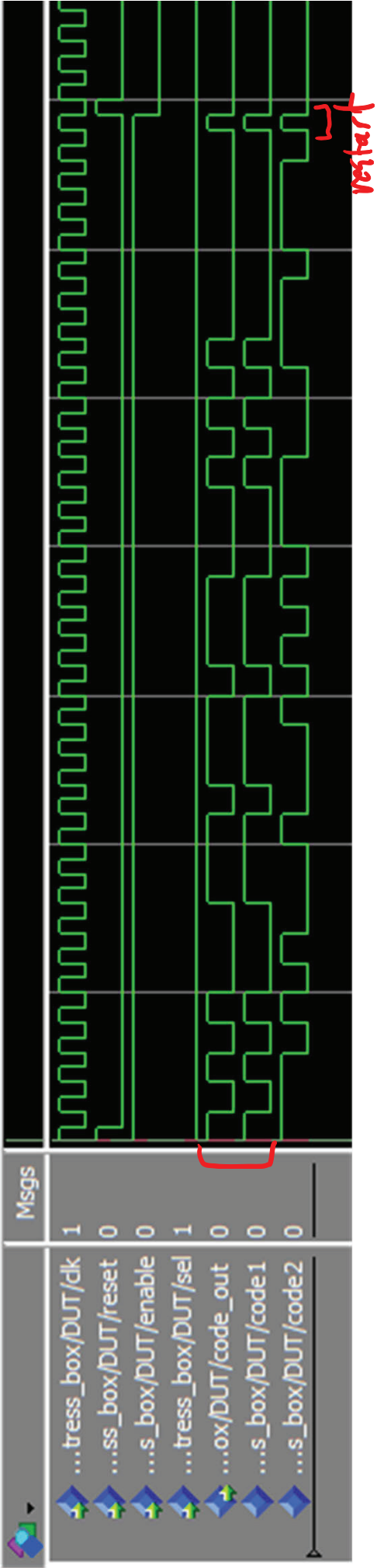

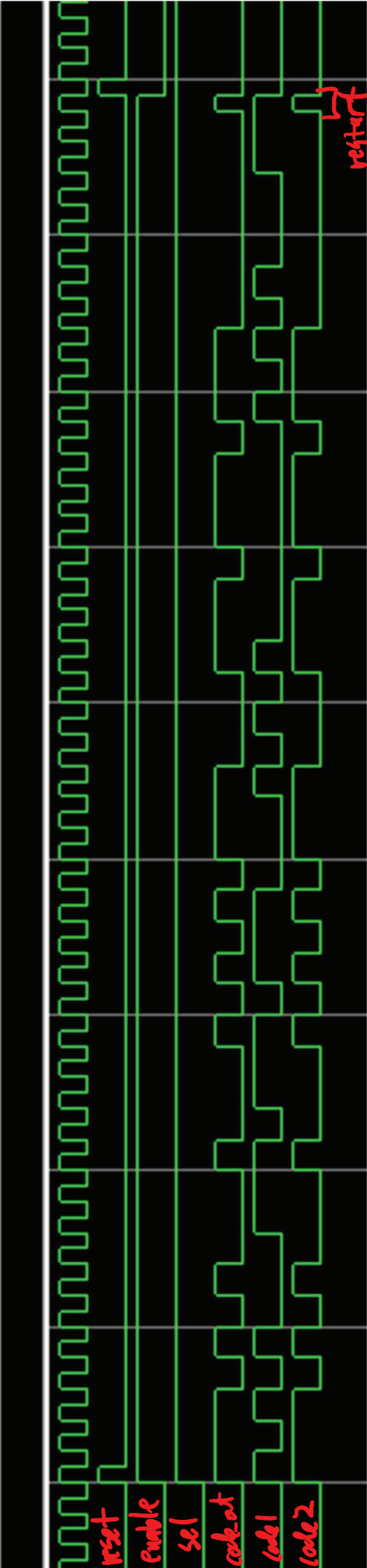In these waveforms, the complete functionality of a distress box is demonstrated. Initially, with sel set to 0, the box transmits SOS in morse code. As such, code1, which corresponds to the SOS box, is copied to code_out. The box begins to restart the transmission before we disable transmission by setting enable to 0.



Next, the box is reset and reenabled, and we switch from SOS mode to DEVO mode by switching sel to 1. This means code2 is copied to code_out, which produces the morse code for DEVO. Similar behaviour to the above waveform is exhibited: it begins a retransmission before we disable transmission.

Discussion:

The “box” component is a generic binary signal repeater, which can be customized to support any signal pattern consisting of binary 1/0 values by way of generic map. It has clk, reset, and enable inputs. Reset initializes the box to the beginning of the signal pattern, and on each rising edge of clk, it steps to the next unit of the signal pattern. If enable is set to 0, no output is produced, and the box holds its output to 0. The signal is generated by connecting a sequencer (which decrements its way through states, and underflows to the beginning of the sequence once it hits zero) to a decoder (which can interpret the states generated by the sequencer and produce either a 1 or a zero, depending on the current state and the given signal pattern).

The distress box incorporates two instances of morse code signal generators; one for “SOS” and one for “DEVO”. Each box is defined in terms of generic values, so the same component can be used for both generators. When instantiating the two boxes, all we have to do is pass the data width, length of our signal, and a `std_logic_vector` containing our desired signal via generic map. These generators have built-in support for enable/disable and asynchronous reset functionality, and require a clock signal to function. These signals are directly mapped to the enable, reset, and clk inputs of the distress box.

The distress box also implements additional functionality: a selection switch by way of which the user may choose whether they want to generate a SOS signal or a DEVO signal, which is accomplished by a simple multiplexer. The final waveform is sent to the `code_out` output of the distress box.